



信息科学与技术学院

School of Information Science and Technology

# CS 110

# Computer Architecture

# Digital Circuits and Systems

**Instructors:**

**Siting Liu & Chundong Wang**

Course website: [https://toast-](https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/Spring-2024/index.html)

[lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/Spring-2024/index.html](https://toast-lab.sist.shanghaitech.edu.cn/courses/CS110@ShanghaiTech/Spring-2024/index.html)

**School of Information Science and Technology (SIST)**

**ShanghaiTech University**

2024/3/28

# Administratives


- Lab 5 will be available, please prepare in advance!
- HW 3 will be available soon, ddl April 9th, start early!
- Proj1.1 ddl approaching, April 8th
- Proj1.2 will be released next week
- Future discussion (teaching center 301) schedule:
  - This Friday (Mar. 29th) on CALL/RISC-V, useful for Proj1.1, covered by TA Chen Suting.
  - Next Monday (April 1st) on CALL and digital circuit basics covered by TA Chen Suting and Yang Chao.
  - Next Friday (April 5th) no discussion (QingMing holiday).
  - April 7th (班) discussion on digital circuit basics by TA Yang Chao.
  - April 8th (tentative mid-term I in that week), mid-term review by Yang Chao.
  - After that, the same content for Friday and the next Monday.

# Outline

- Digital system
- Combinational logics
- **State elements**
  - **Flip-flops & registers**
  - **Finite state machine (FSM)**
  - **Timing constraints**
 
# Warm-up

- What does the following logic circuit do? (Select all that apply)





- A. Output 1 if  $a=b=1$
- B. Output 1 if  $b=c=1$
- C. Output 1 if  $a=c=1$
- D. Output 1 if  $a=b=c=1$
- E. Output 1 if at least two of  $a, b, c$  is 1
- F. Output the “majority” bit of  $a, b, c$
- G. None of the above

# Synchronous Digital System (SDS)

- A system that processes digital signals (0s and 1s)
  - Synchronous digital systems consist of two basic types of circuits.
    - Combinational logic circuits
      - The outputs solely depend on the input
      - No way to store information
    - State Elements (**this lecture**)
      - Circuits that store information
      - E.g., **registers** and memory
      - Finite state machine
      - Timing constraints
- Our Goal: Implement a RISC-V processor as a synchronous digital system.
  - This SDS should have the capabilities to execute RISC-V instructions.

 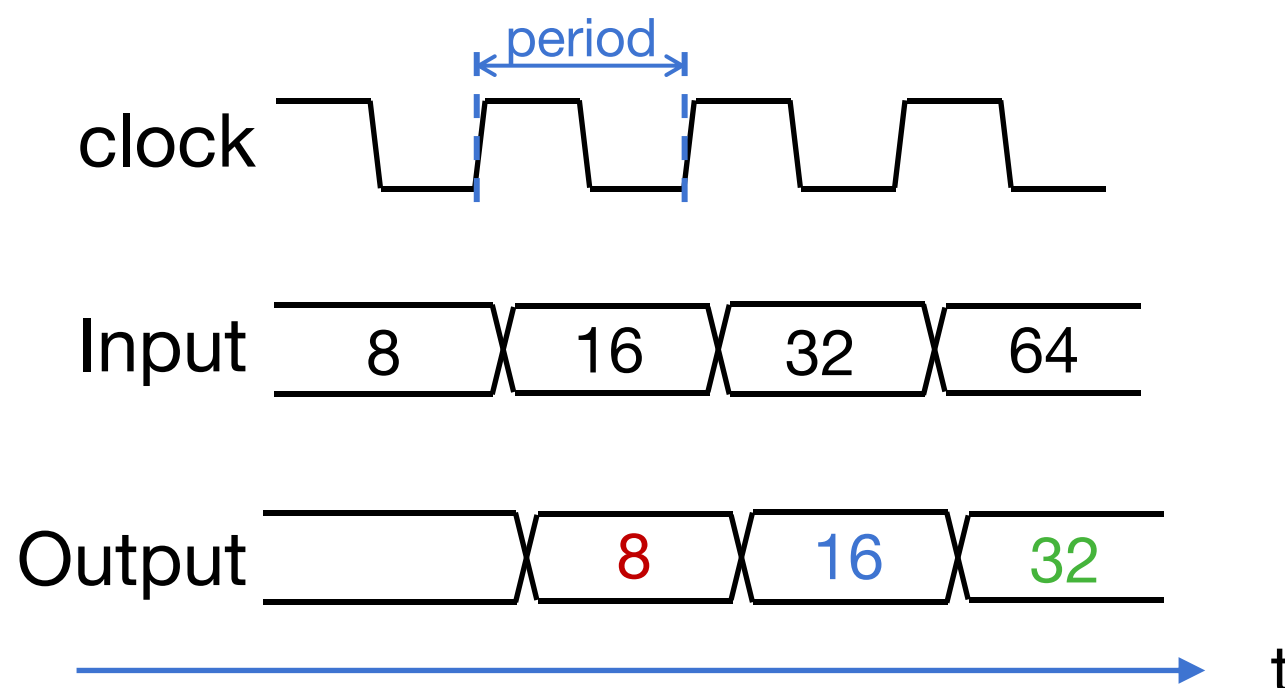
# Registers

- A digital element that can store and hold state
- State change governed by a special signal called “clock” (or trigger)
- Sample input on trigger (can be the positive or negative edge of the clock)  
default in this course
- At all other times, ignore the input
- Output follows the value stored
- **Timing diagram** describes its behavior





 
# Inside a Register

- A register can be implemented by multiple D flip-flops (DFFs)
- Each DFF can store 1 bit (behavior the same as a register)
- Timing diagram



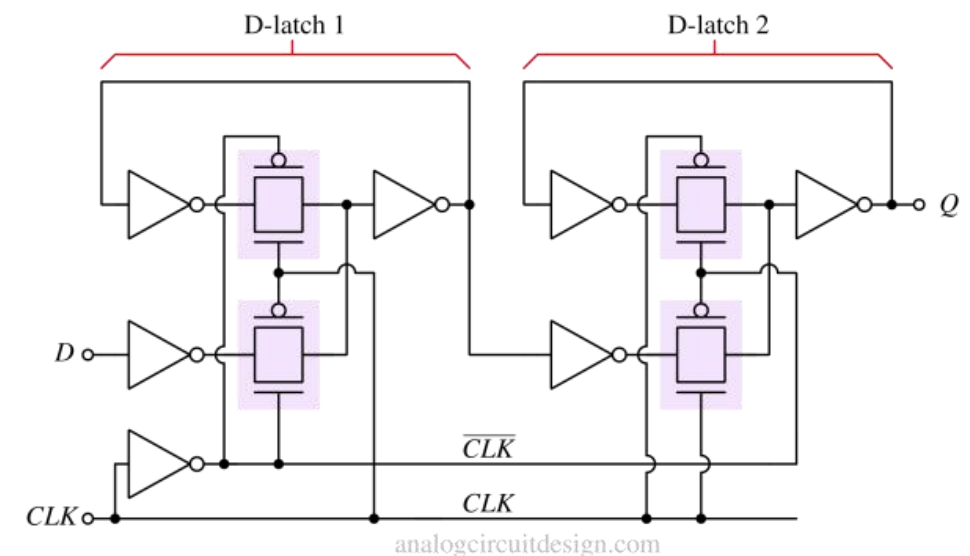  
- The DFFs share one clock signal to **synchronize** n-bit register (a possible implementation)




A possible transistor-level implementation of a DFF (optional)
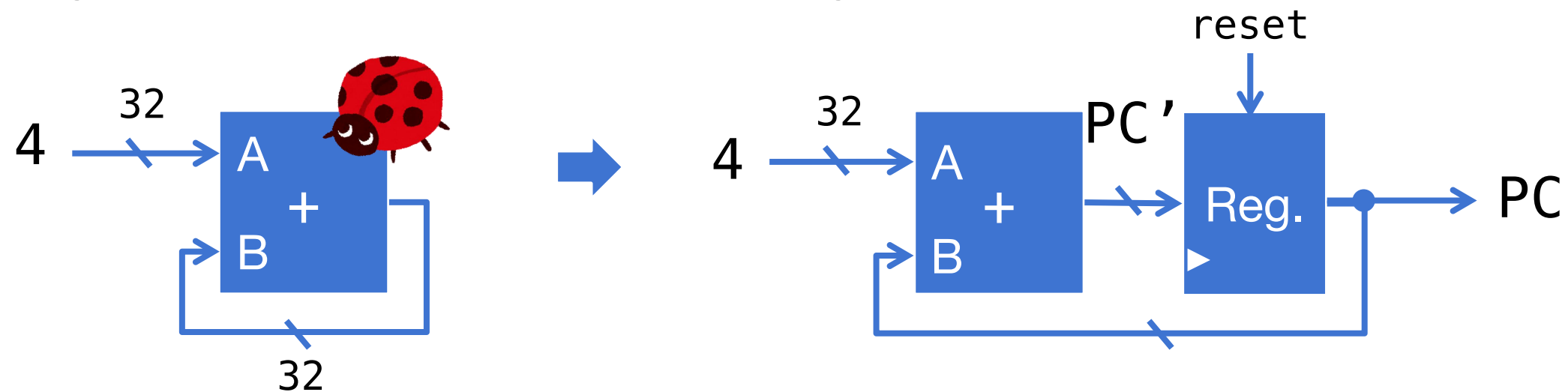
# Combine Combinational Circuits and DFFs

- Synchronous digital circuit can have feedback, e.g., iterative accumulator
  - e.g.  $PC = PC + 4$  without considering branch or jump





- Timing diagram

 



 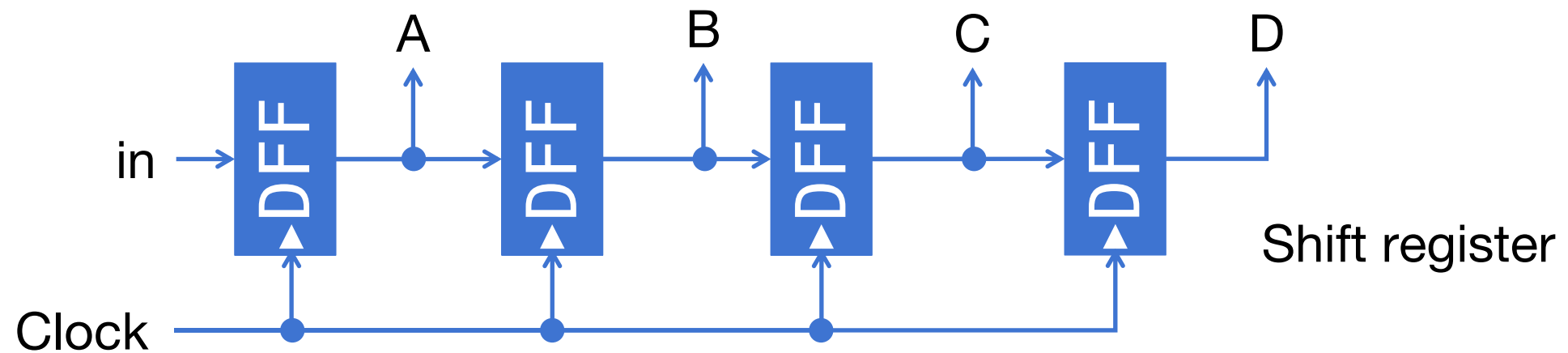
# Combine Combinational Circuits and DFFs

- Synchronous digital circuit that can have multiple stages of DFFs or registers, and **all the registers share one clock**



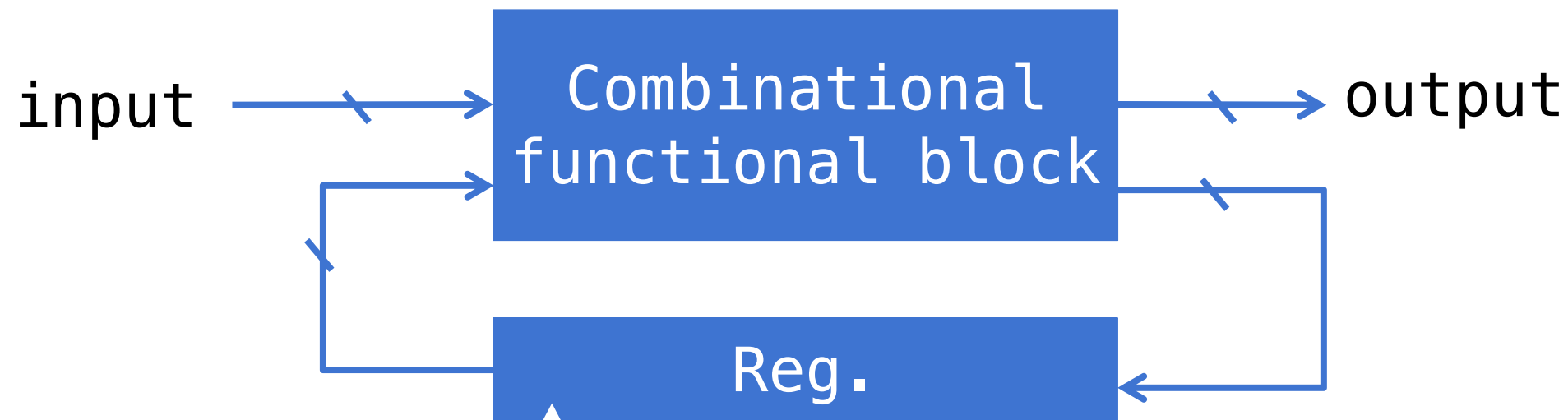
# General form of synchronous circuits

- State element can work together with combinational logic (can have feedbacks)




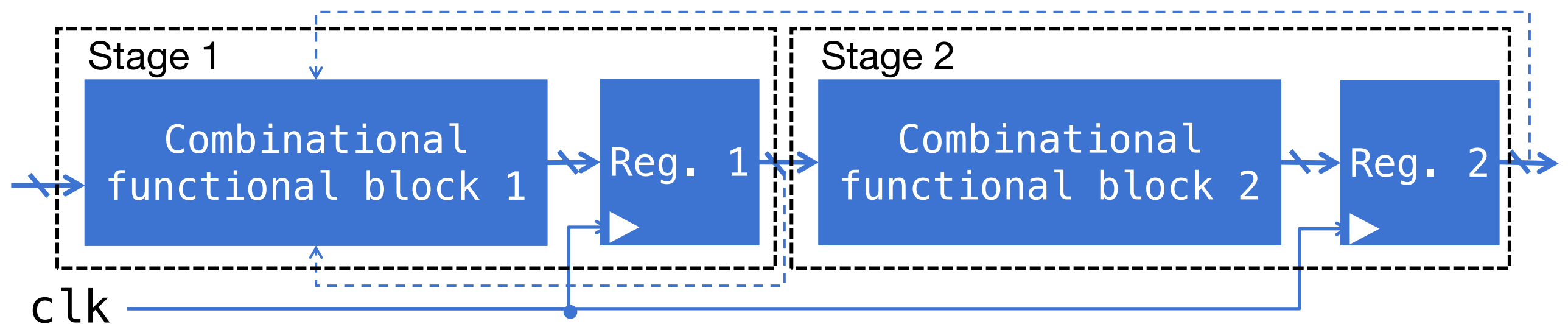- We can cascade multiple stages of the above synchronous circuit (can have feedbacks across stages)


 
# Model of synchronous circuits, FSM

- Finite state machine (FSM): a mathematical model of computation
- It is an abstract machine that can be in exactly one of a finite number of states at any given time.
- The FSM can change from one state to another in response to some inputs; the change from one state to another is called a transition.
- An FSM is defined by a list of its states, its initial state (entrance), the inputs that trigger each transition, and optional outputs



A turnstile


## States

Locked

Unlock

 
# Model of synchronous circuits, FSM

- Finite state machine (FSM): a mathematical model of computation
- It is an abstract machine that can be in exactly one of a finite number of states at any given time.
- The FSM can change from one state to another in response to some inputs; the change from one state to another is called a transition.
- An FSM is defined by a list of its states, its initial state (entrance), the inputs that trigger each transition, and optional outputs



A turnstile

Entrance

 


Locked

Unlock



 
# Model of synchronous circuits, FSM

- Finite state machine (FSM): a mathematical model of computation
- It is an abstract machine that can be in exactly one of a finite number of states at any given time.
- The FSM can change from one state to another in response to some inputs; the change from one state to another is called a transition.
- An FSM is defined by a list of its states, its initial state (entrance), the inputs that trigger each transition, and optional outputs




A turnstile

 

 
# Model of synchronous circuits, FSM

- Finite state machine (FSM): a mathematical model of computation
- It is an abstract machine that can be in exactly one of a finite number of states at any given time.
- The FSM can change from one state to another in response to some inputs; the change from one state to another is called a transition.
- An FSM is defined by a list of its states, its initial state (entrance), the inputs that trigger each transition, and optional outputs




A turnstile

 



 
# Model of synchronous circuits, FSM

- Define: State “Locked/hold the bar” as ‘0’, “Unlock/release the bar” as ‘1’; use register/DFF to store the state
- Define: “valid payment” as input ‘1’, “invalid payment” as input ‘0’
- Build a synchronous circuit that implements automatic control of the turnstile




A turnstile

 

# Model of synchronous circuits, FSM

- Define: State “Locked/hold the bar” as ‘0’, “Unlock/release the bar” as ‘1’; use register/DFF to store the state
- Define: “valid payment” as input ‘1’, “invalid payment” as input ‘0’
- Build a synchronous circuit that implements automatic control of the turnstile
- Truth table of this synchronous circuit

input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1

 

$Q_{k-1}$ : state at the (k-1)th clock cycle  
 $Q_k$ : state at the (k)th clock cycle




# Model of synchronous circuits, FSM

- Define: State “Locked/hold the bar” as ‘0’, “Unlock/release the bar” as ‘1’; use register/DFF to store the state
- Define: “valid payment” as input ‘1’, “invalid payment” as input ‘0’
- Build a synchronous circuit that implements automatic control of the turnstile
- Truth table of this synchronous circuit

input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1

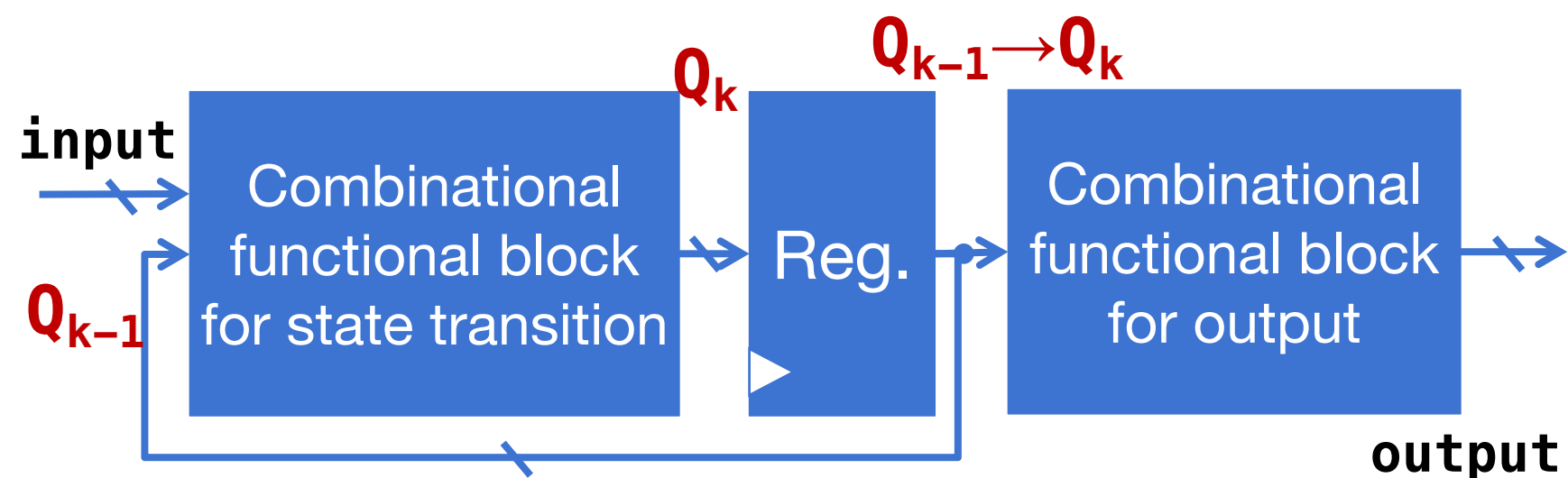Template of a synchronous circuit that implements the FSM




$Q_{k-1}$ : state at the (k-1)th clock cycle

$Q_k$ : state at the (k)th clock cycle


# Model of synchronous circuits, FSM

- Timing diagram (general case)

 

input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1

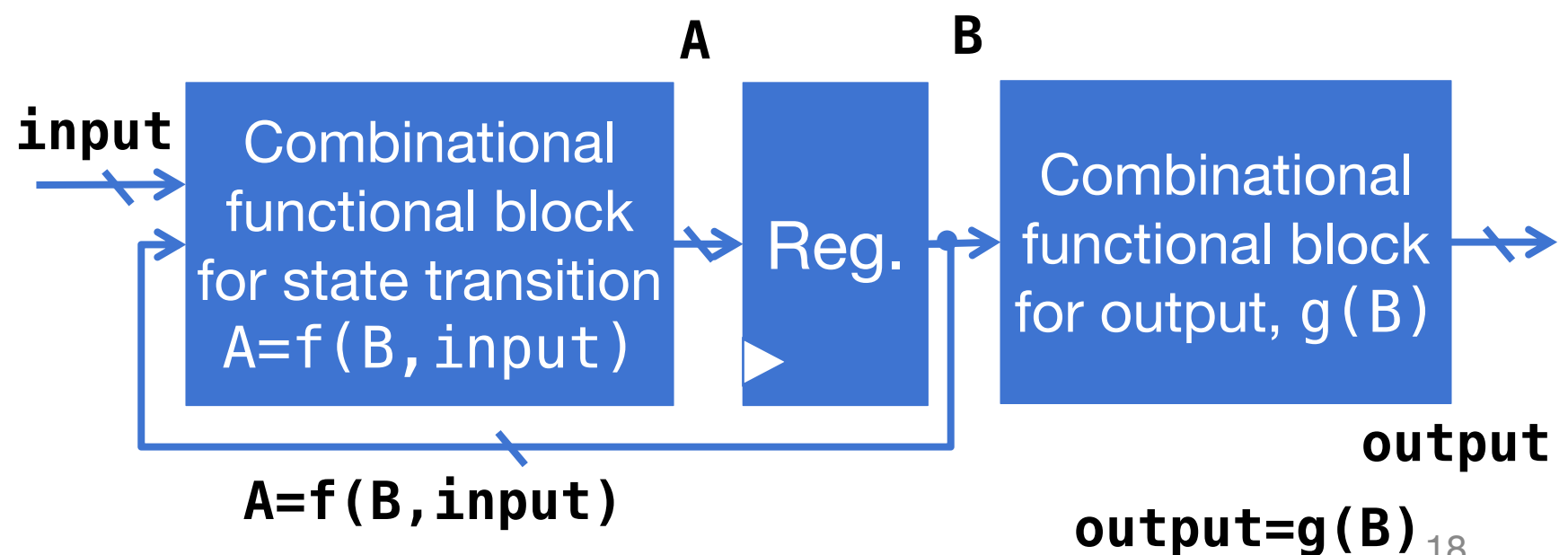Template of a synchronous circuit that implements the FSM



# Model of synchronous circuits, FSM

- Build the circuits

input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1


State transition logic

$$Q_k = f(\text{input}, Q_{k-1})$$



$$Q_k = \text{input}$$

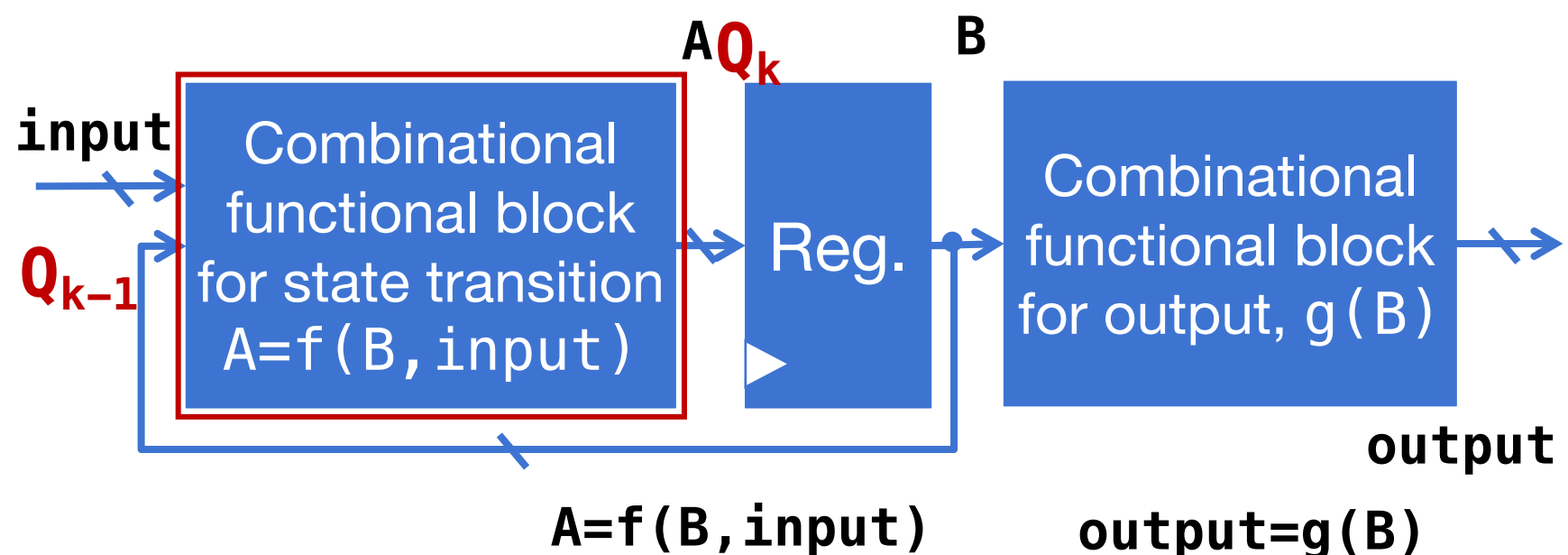Template of a synchronous circuit that implements the FSM



# Model of synchronous circuits, FSM

- Build the circuits

input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1


Output logic

$$\text{Output} = g(Q_k)$$



$$\text{Output} = Q_k$$

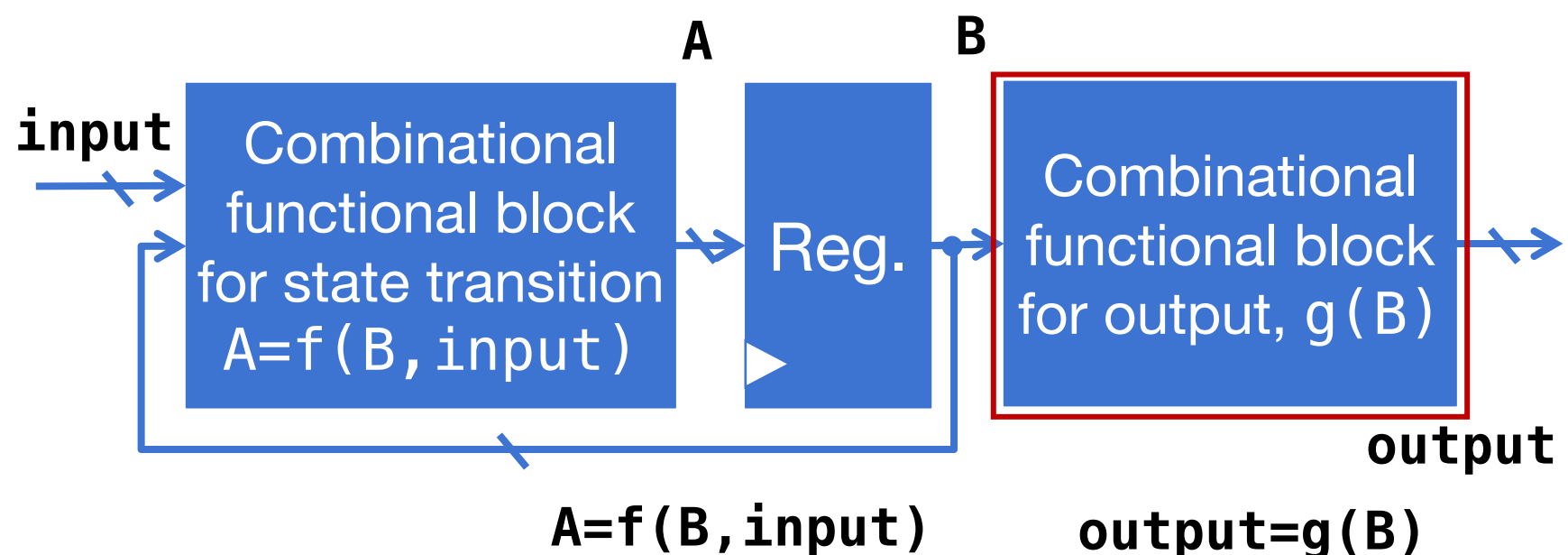
Template of a synchronous circuit that implements the FSM




# Model of synchronous circuits, FSM

- Build the circuits

input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1

 

# Model of synchronous circuits, FSM

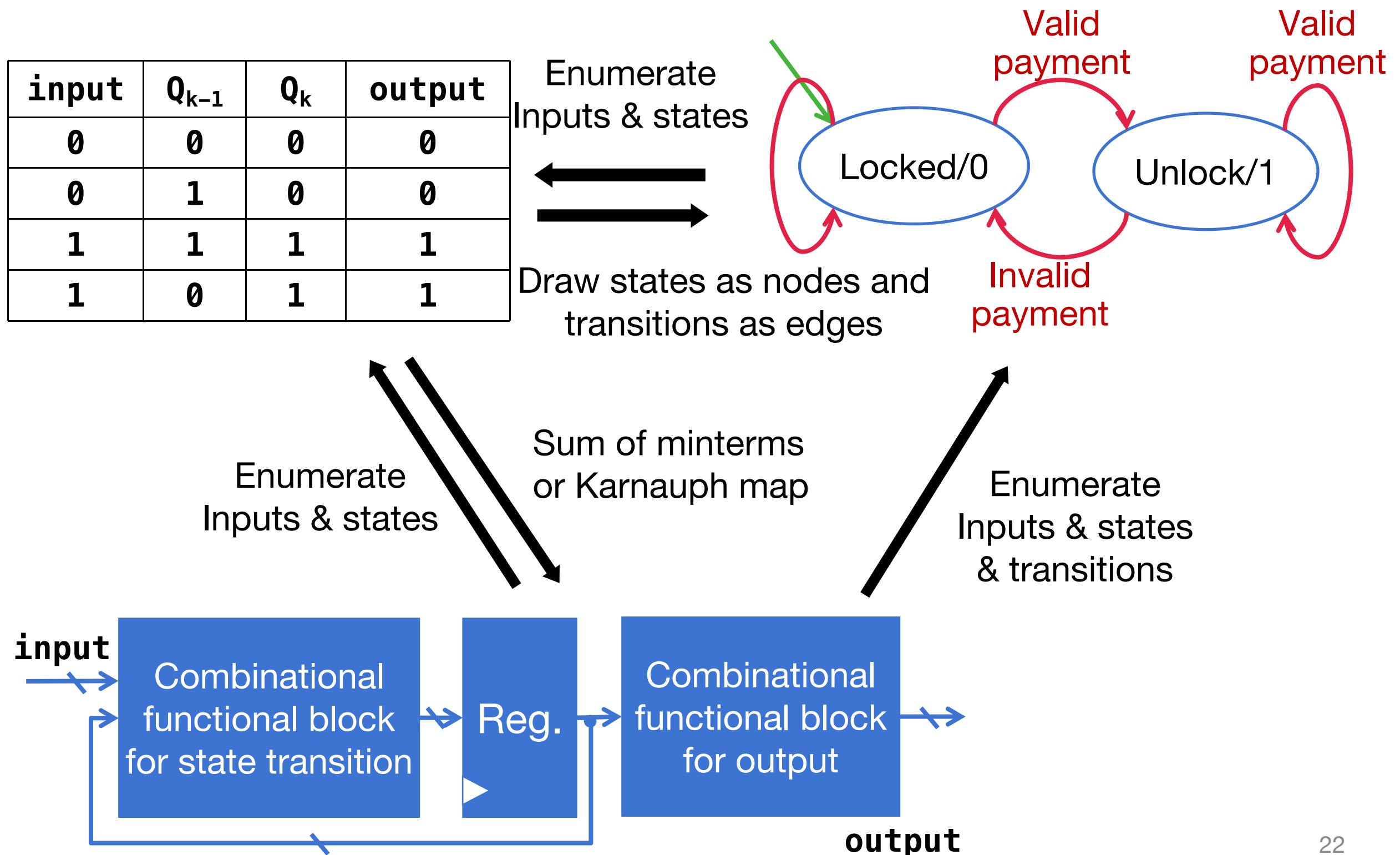

# Moore machine vs. Mealy machine


- Moore machine

input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1

Enumerate  
Inputs & states



 
Draw states as nodes and  
transitions as edges



Sum of minterms  
or Karnaugh map

Enumerate  
Inputs & states

 - Output depends solely on the current state
- Output controlled by the clock somewhat




# Moore machine vs. Mealy machine

- Mealy machine


input	$Q_{k-1}$	$Q_k$	output
0	0	0	0
0	1	0	0
1	1	1	1
1	0	1	1

Enumerate  
Inputs & states

 

Enumerate  
Inputs & states

Sum of minterms  
or Karnaugh map

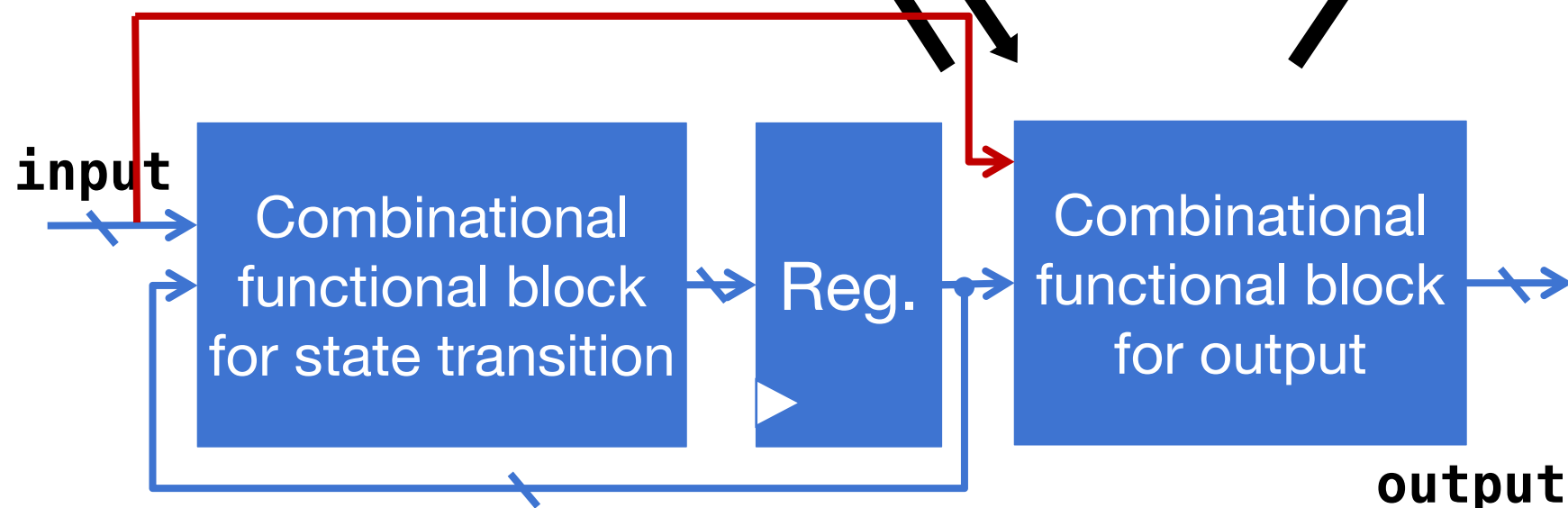

- Output depends on both the current state **and** input
- Output uncontrolled by the clock
- Mealy and Moore machines are interchangeable
- Mealy and Moore outputs can co-exist in one synchronous circuit




# Summary for building synchronous circuits


- Step 1: Draw finite state machine of the desired function (we ignore the initialization)
- Step 2: Define/assign binary numbers to represent the states, the inputs and the outputs
- Step 3: Write down the truth table (enumerate input/previous state (and current state) and their corresponding current state (and output))
- Step 4: Use template and decide the combinational block for state transition and output logic
- Otherwise, we can also use simple synchronous circuit blocks to build larger synchronous circuit like for the multi-bit adder
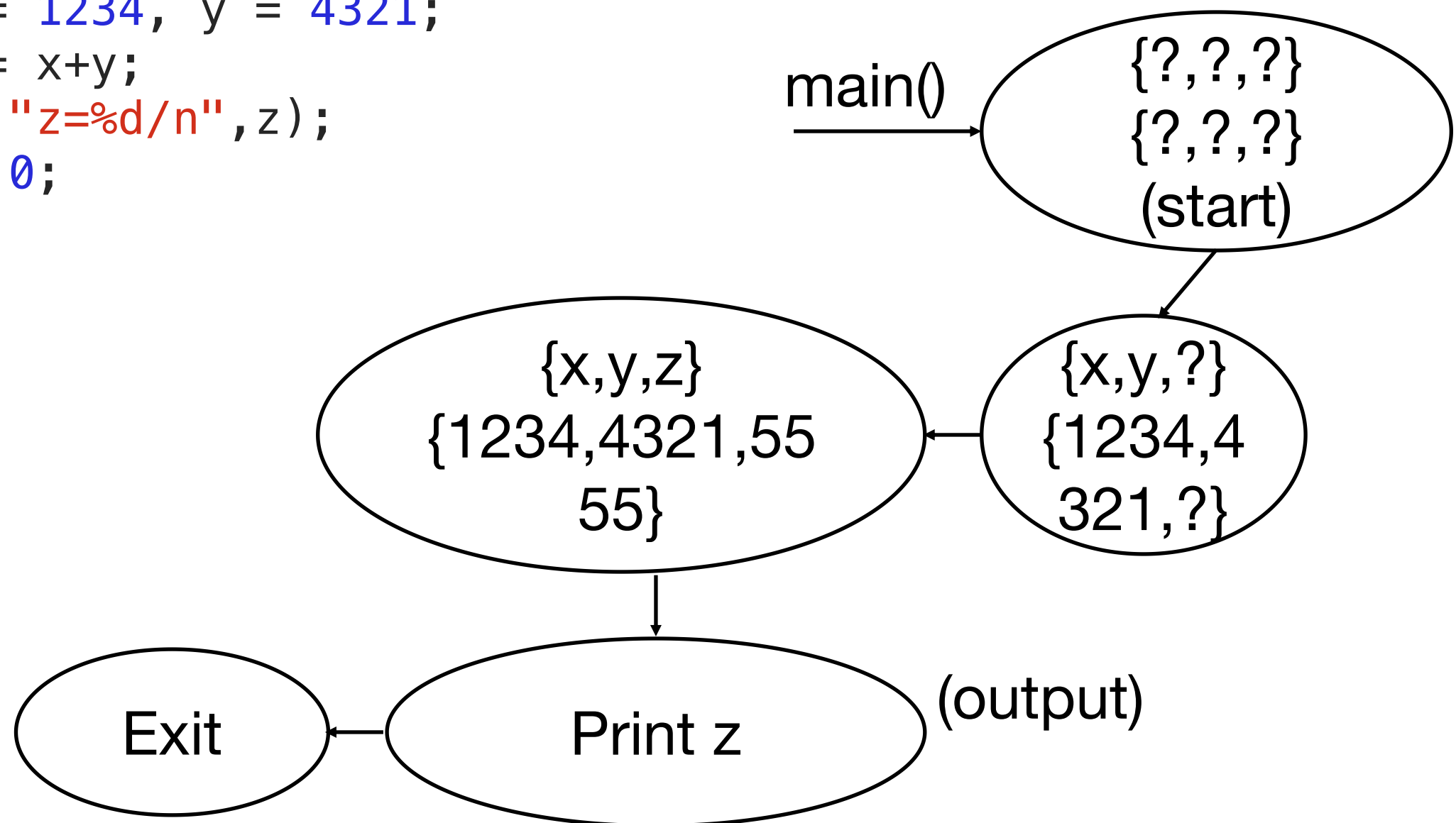
# C Program as an FSM

```
#include <stdio.h>
int main() { //compute 1234 + 4321
    int x = 1234, y = 4321;
    int z = x+y;
    printf("z=%d/n", z);
    return 0;
}
```




# ISA as an FSM

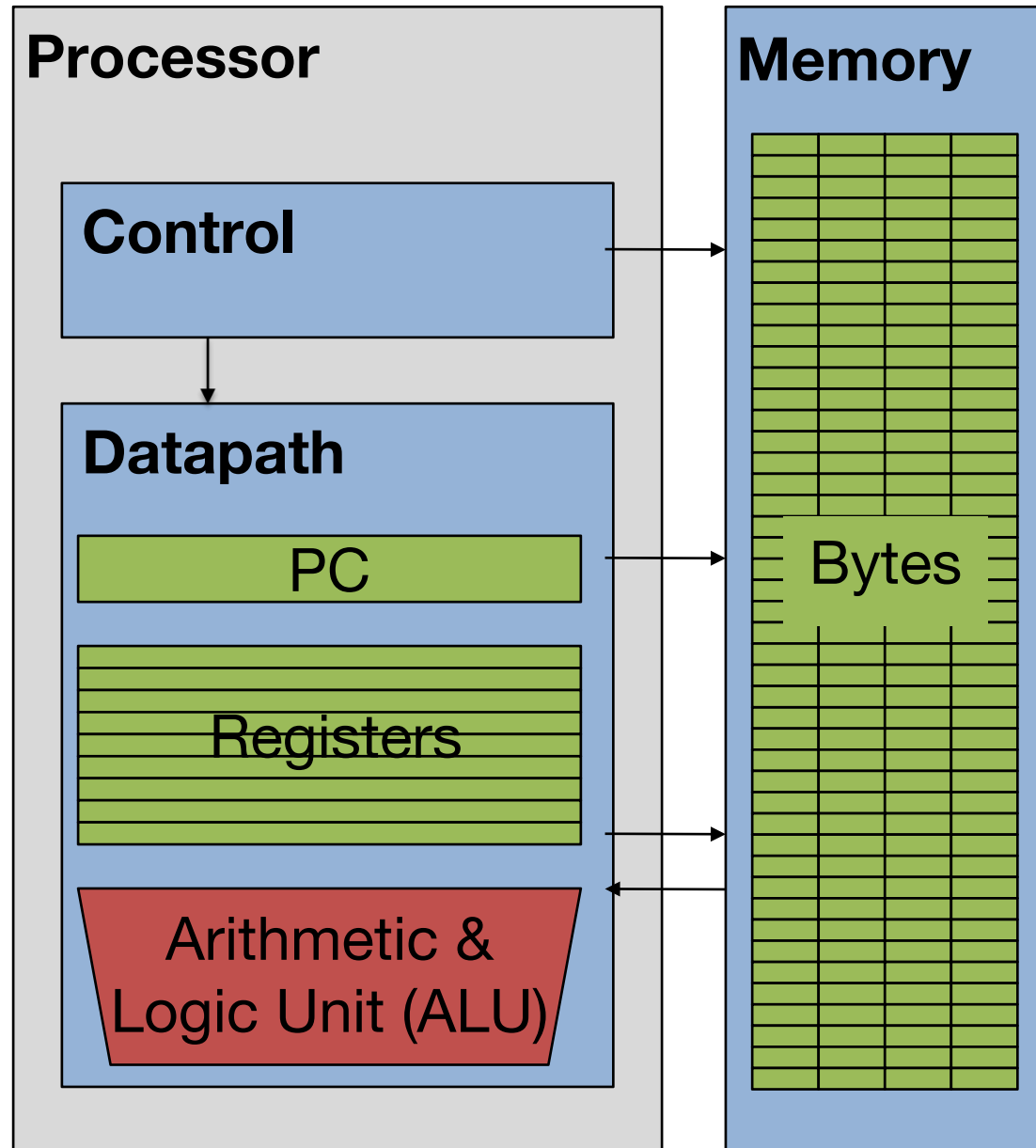

- States: all registers & memory
- Transition: register/memory value change
- Entrance: power on/reset
- Input: instructions, can change registers/memory value
 
# Timing in synchronous circuits

- Can the frequency of the clock be infinity?



DFFs require a time window to correctly capture a signal, i.e., the signal should be stable during this time window

**Setup time:** the period that the input should be ready before the edge


Time window

**Hold time:** the period that the input should hold its value after the edge

C


D

Q

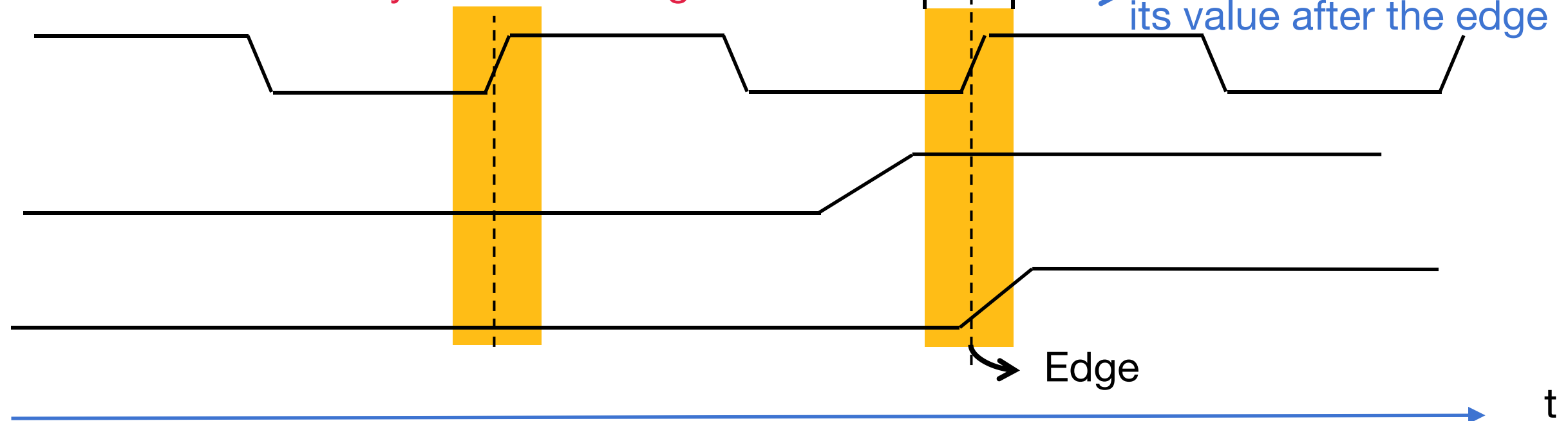

 
# Timing in synchronous circuits


- DFF also has delay:  $t_{\text{clk-to-Q}}$



 
DFFs require a time window to correctly capture a signal, i.e., the signal should be stable during this time window




# Estimating the max frequency

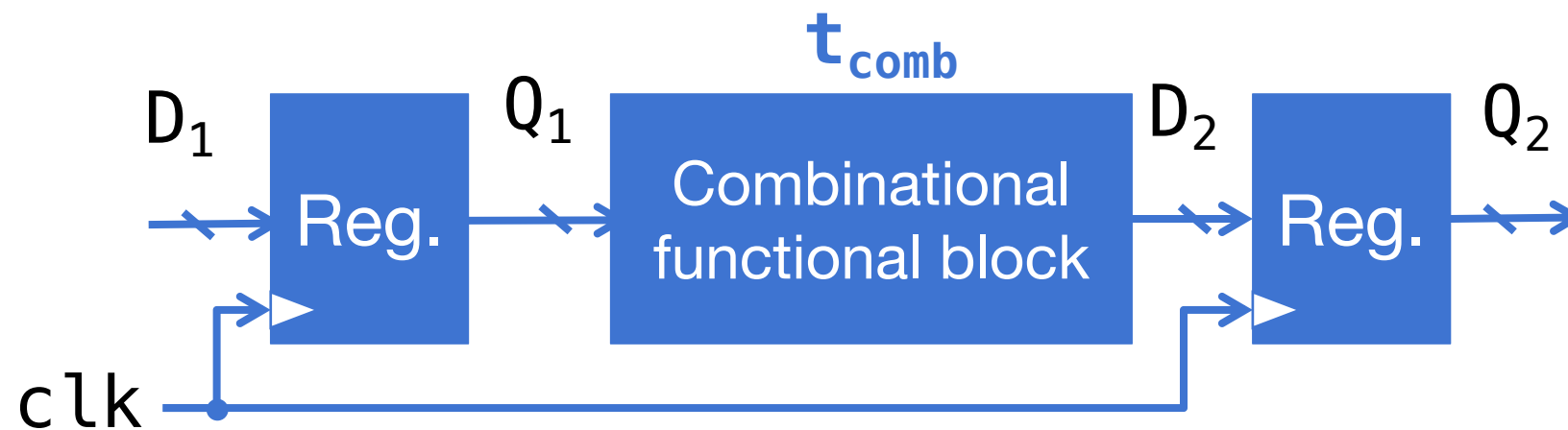

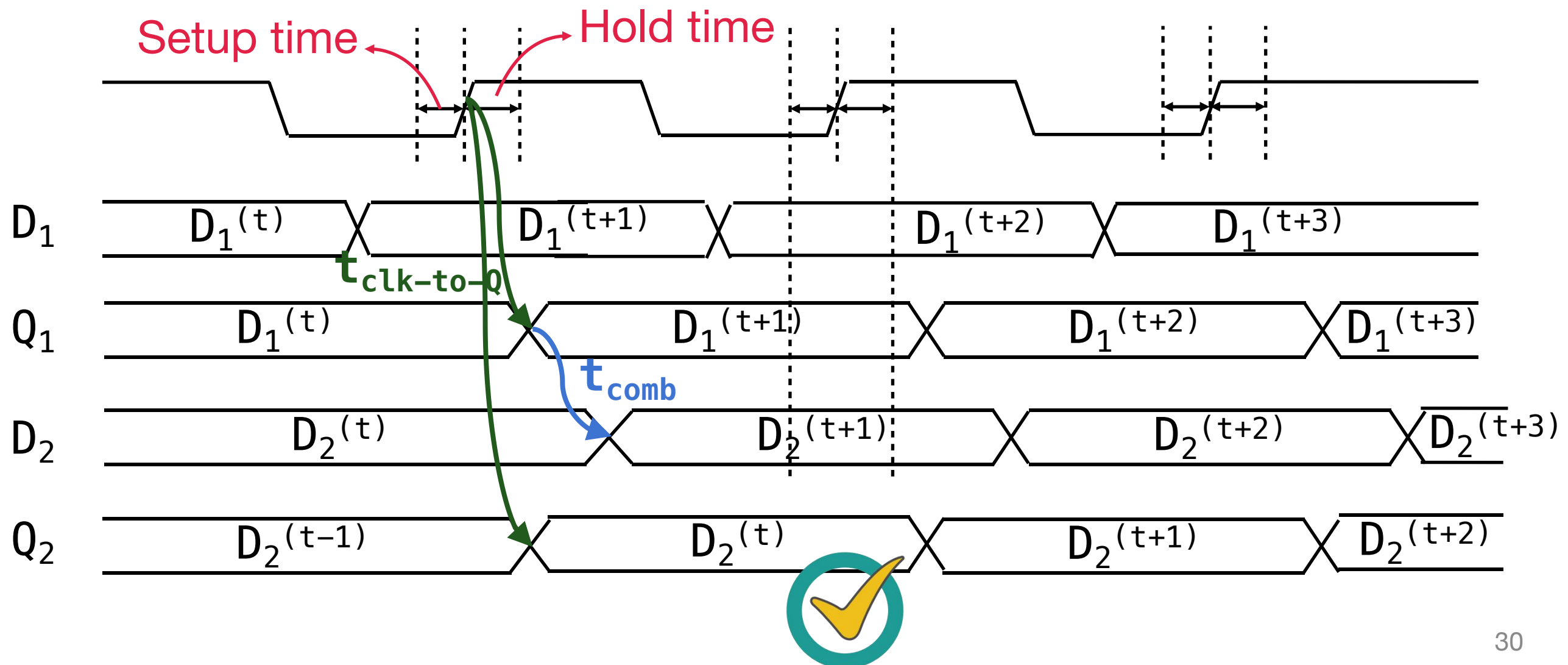
Typical digital system: a mix of combinational circuits & registers



# Estimating the max frequency

 

 Typical digital system: a mix of combinational circuits & registers




# Estimating the max frequency

Max frequency =  $1/\text{min clock period}$

$$t_{\text{clk-to-Q}} + t_{\text{comb}} \leq \text{min clock period} - \text{setup time}$$

 
Signal  $D_2^{(t+1)}$  should arrive **before** the setup time window




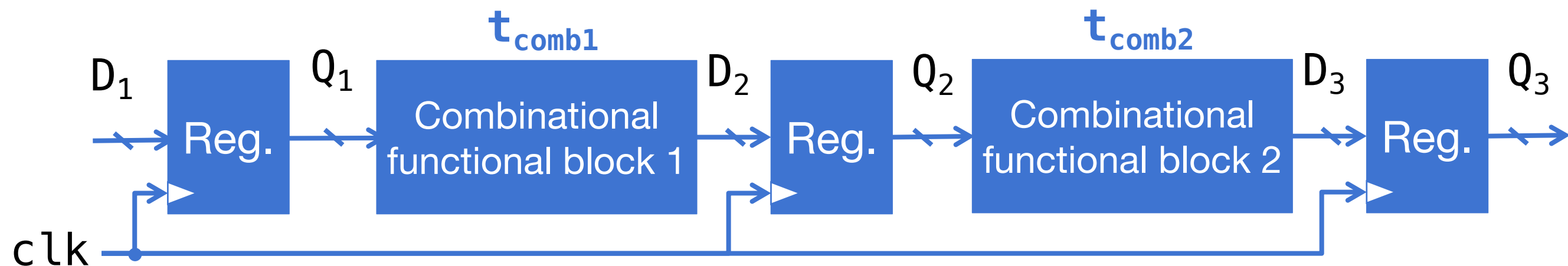
# Clarifications


- A synchronous circuit may contain multiple stages of combinational-block-and-register, while the slowest path decide the max frequency.
- The corresponding path is also called **critical path**.



$$t_{\text{clk-to-Q}} + t_{\text{comb}} \leq \text{min clock period} - \text{setup time}$$

- We simplify the model, so that hold time is not considered. There would also be hold time violation due to some signals changing too fast, but it is not related to the calculation of max frequency of a circuit.

# Question (Your turn)

 

Given	
Clock->Q	1ns
Setup	1ns
Hold	1ns
AND delay	1ns

What is maximum clock frequency?

- A: 5 GHz
- B: 500 MHz
- C: 200 MHz
- D: 250 MHz
- E: 1/6 GHz