



Datapath

Discussion 8

CS110




Yutong Wang

4/12/2024


CAS4ET Lab




Datapath Components

 


Adder

 


Multiplexer

 


ALU

 

register

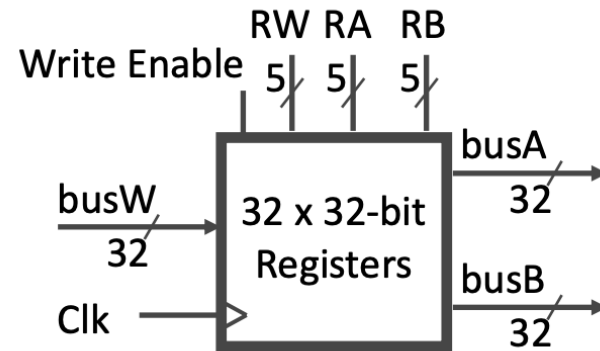

register file

 


memory



5 Stages of Datapath




 - **IF**: Instruction **F**etch
- **ID**: Instruction **D**ecode
- **EX**: **E**xecute
- **MEM**: **M**emory
- **WB**: **W**rite **B**ack




R-format: add

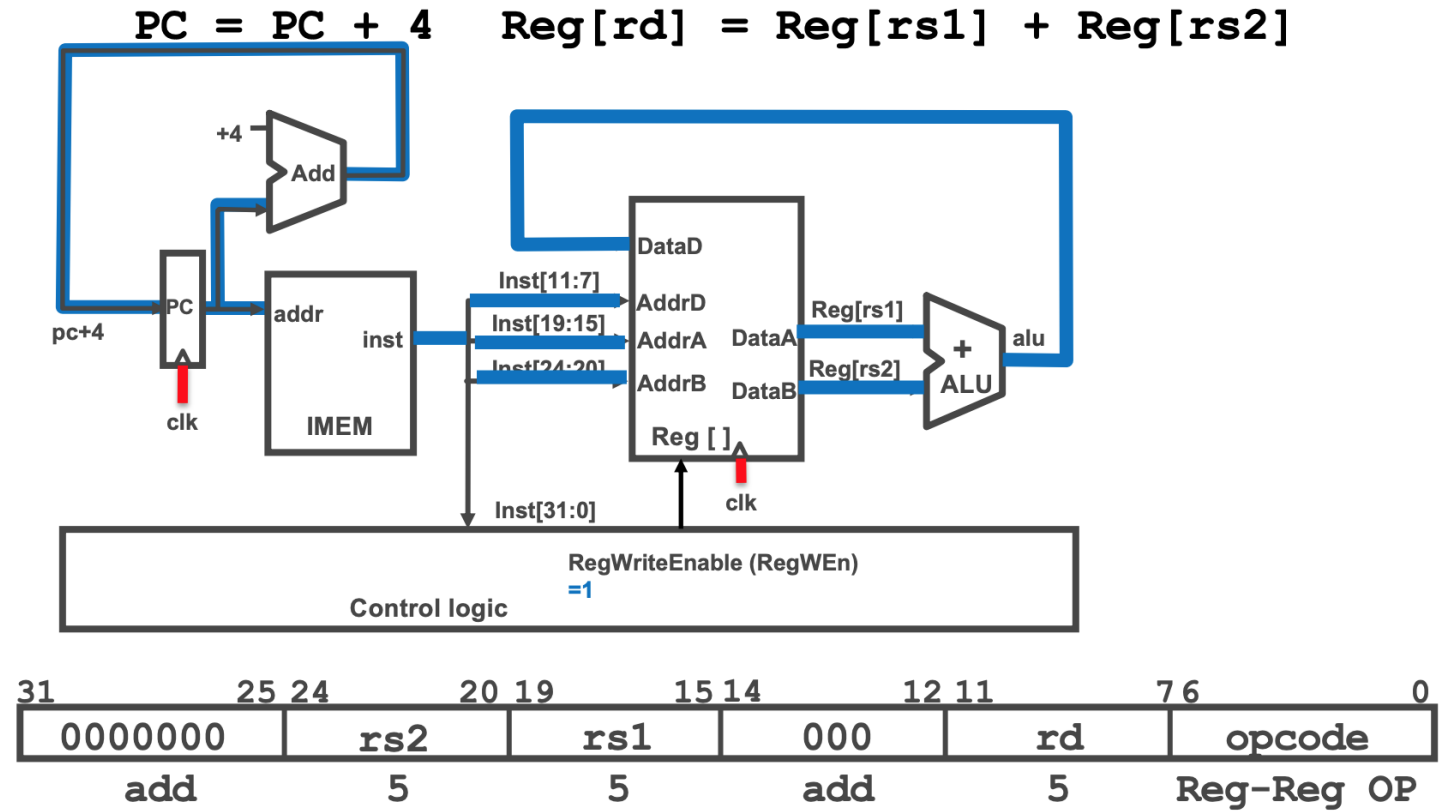- IF
- ID
- **EX**: $alu = R[rs1] + R[rs2]$
- ~~MEM~~
- **WB**: $R[rd] = alu$
- $PC = PC + 4$



Time Diagram

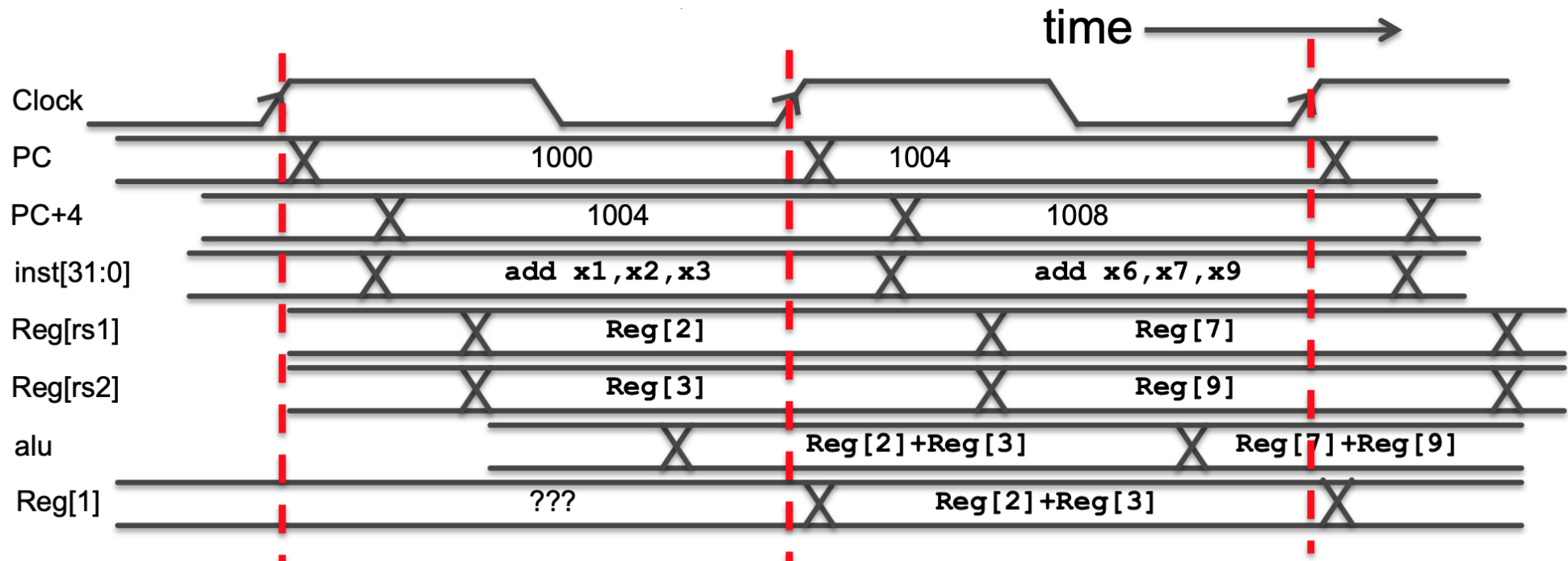


Attention! **WB** actually finishes after the next rising edge of Clock.



I-format: addi



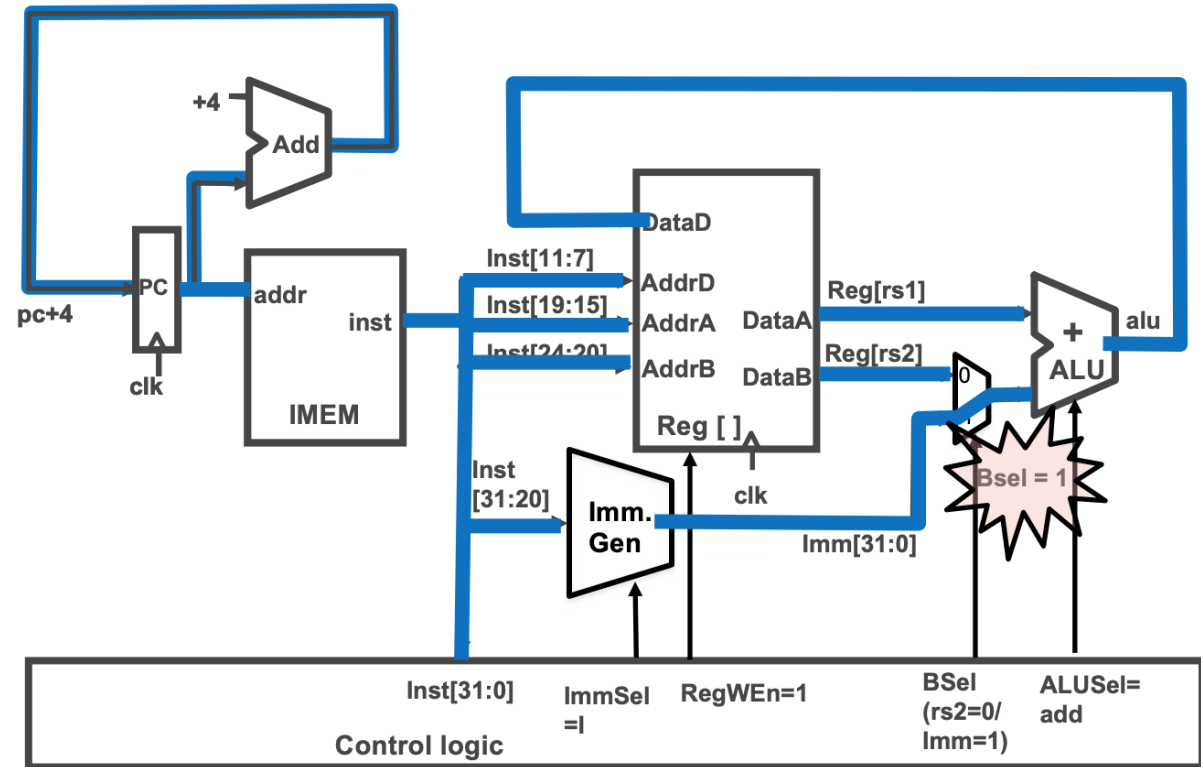
- IF
- ID
- **EX**: $\text{alu} = R[\text{rs1}] + \text{imm}$
- ~~MEM~~
- **WB**: $R[\text{rd}] = \text{alu}$
- $\text{PC} = \text{PC} + 4$



I-format: lw



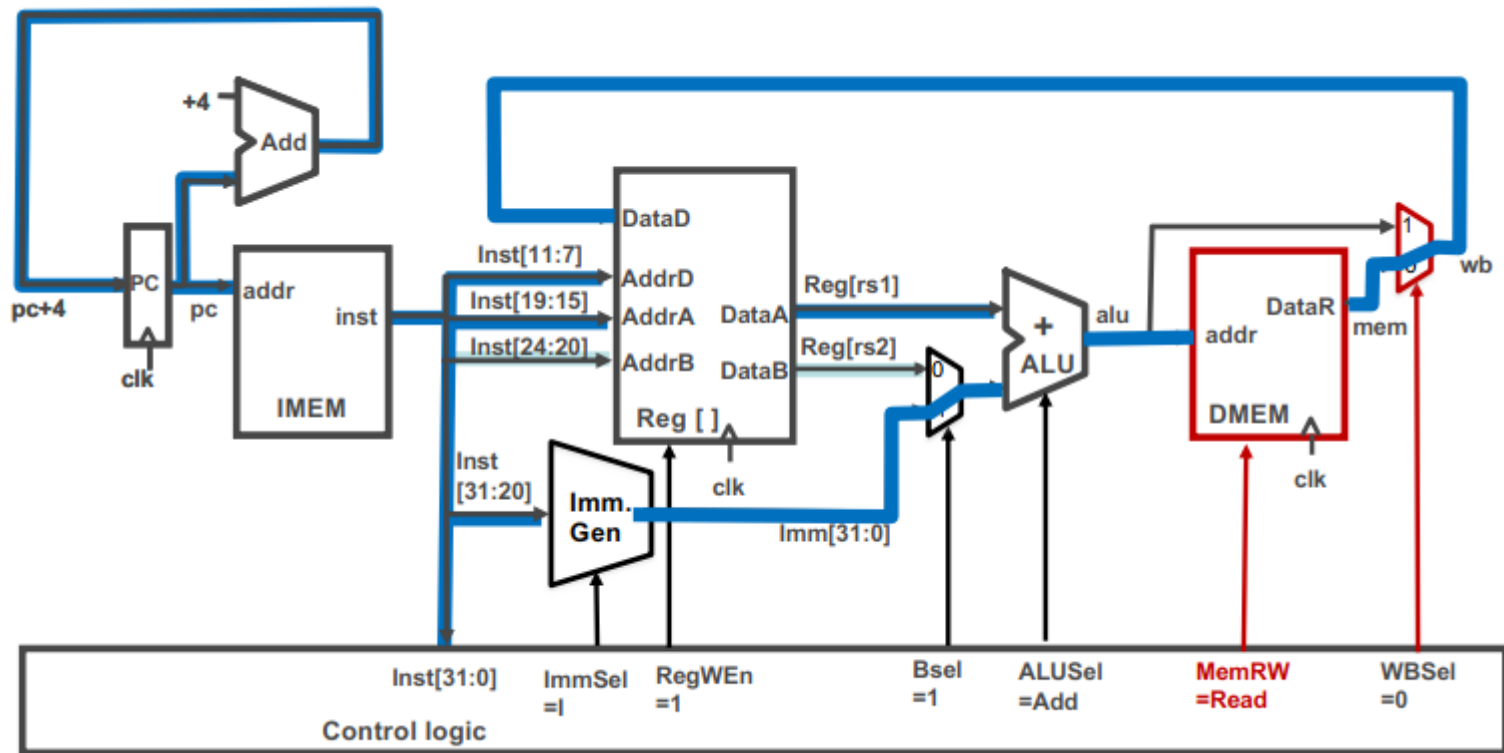
- IF
- ID
- EX: $alu = R[rs1] + imm$
- MEM: $mem = M[alu]$
- WB: $R[rd] = mem$
- $PC = PC + 4$



S-format: sw



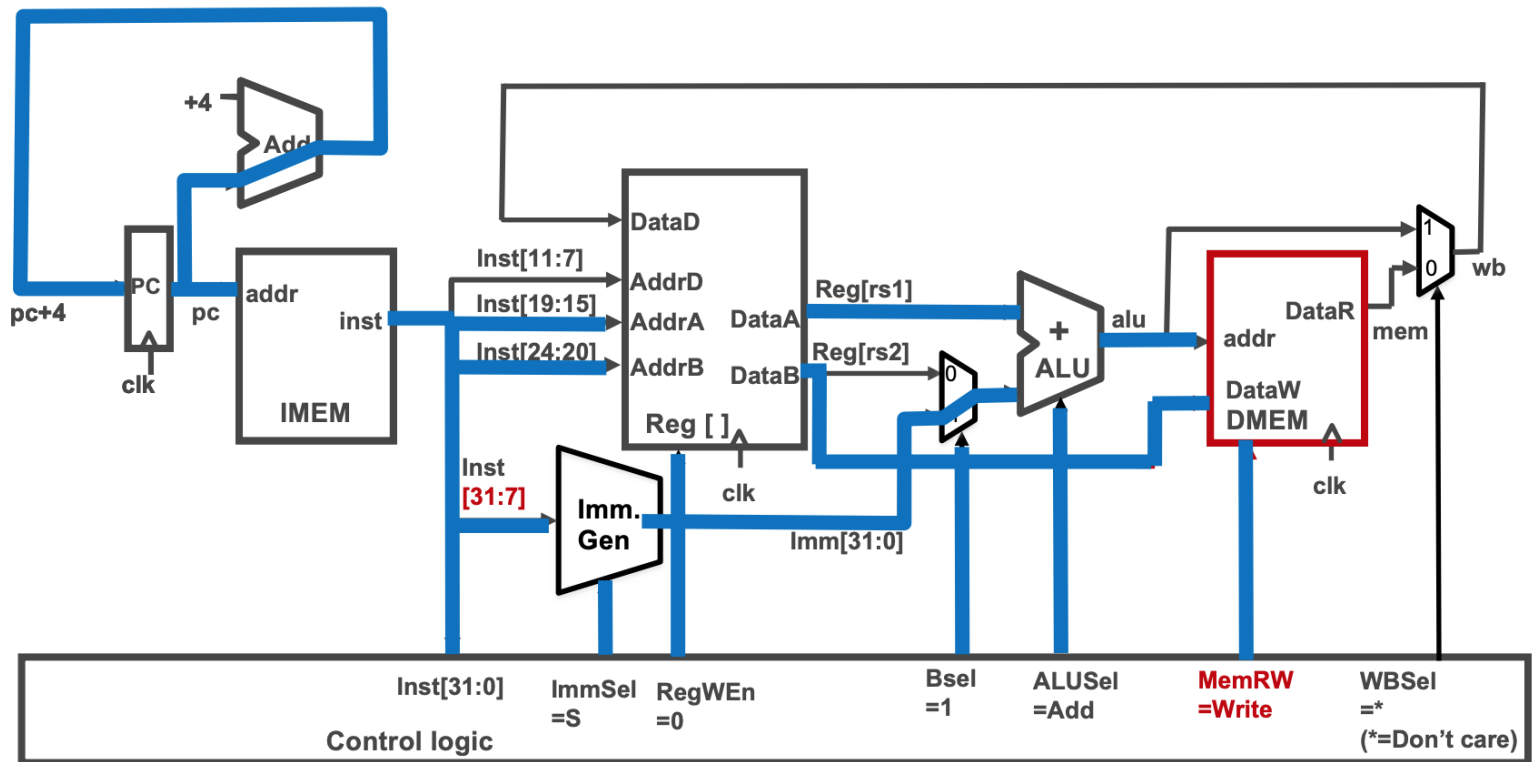
- IF
- ID
- EX: $alu = R[rs1] + imm$
- MEM: $M[alu] = R[rs2]$
- ~~WB~~
- $PC = PC + 4$




B-format



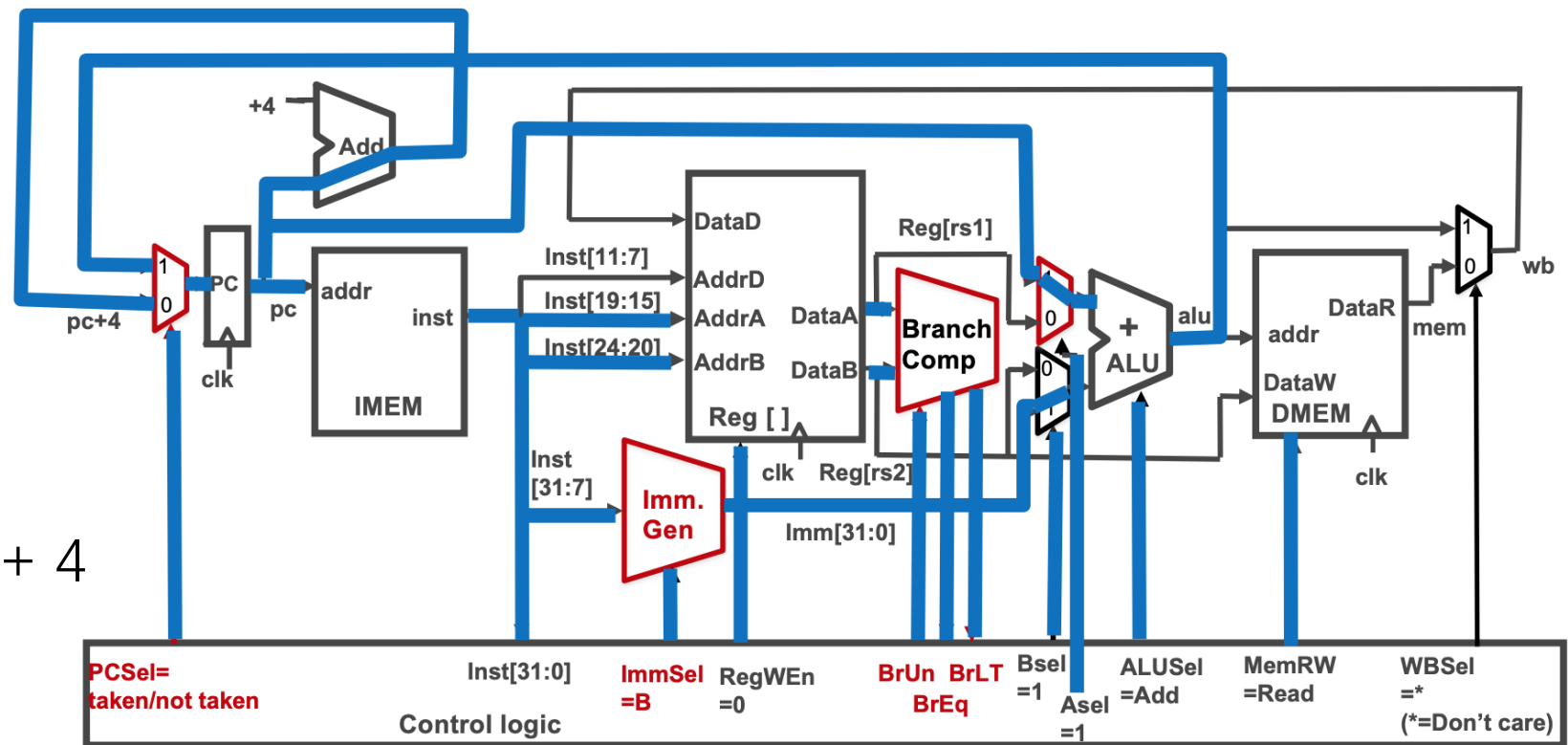
- IF
- ID
- EX: $alu = PC + imm$
- ~~MEM~~
- ~~WB~~
- $PC = PCSel ? alu : PC + 4$



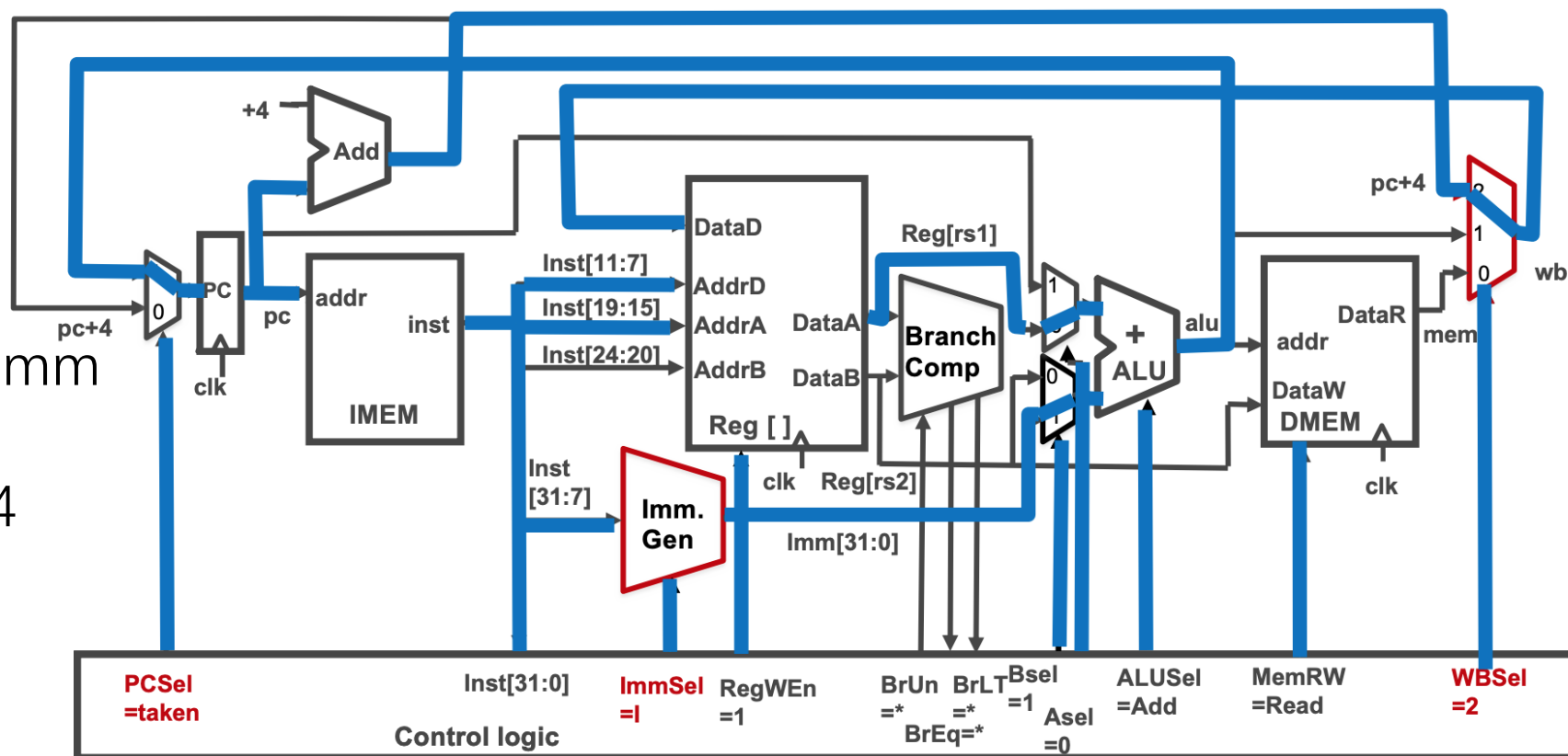- IF
- ID
- EX: $alu = R[rs1] + imm$
- ~~MEM~~
- WB: $R[rd] = PC + 4$
- $PC = alu$




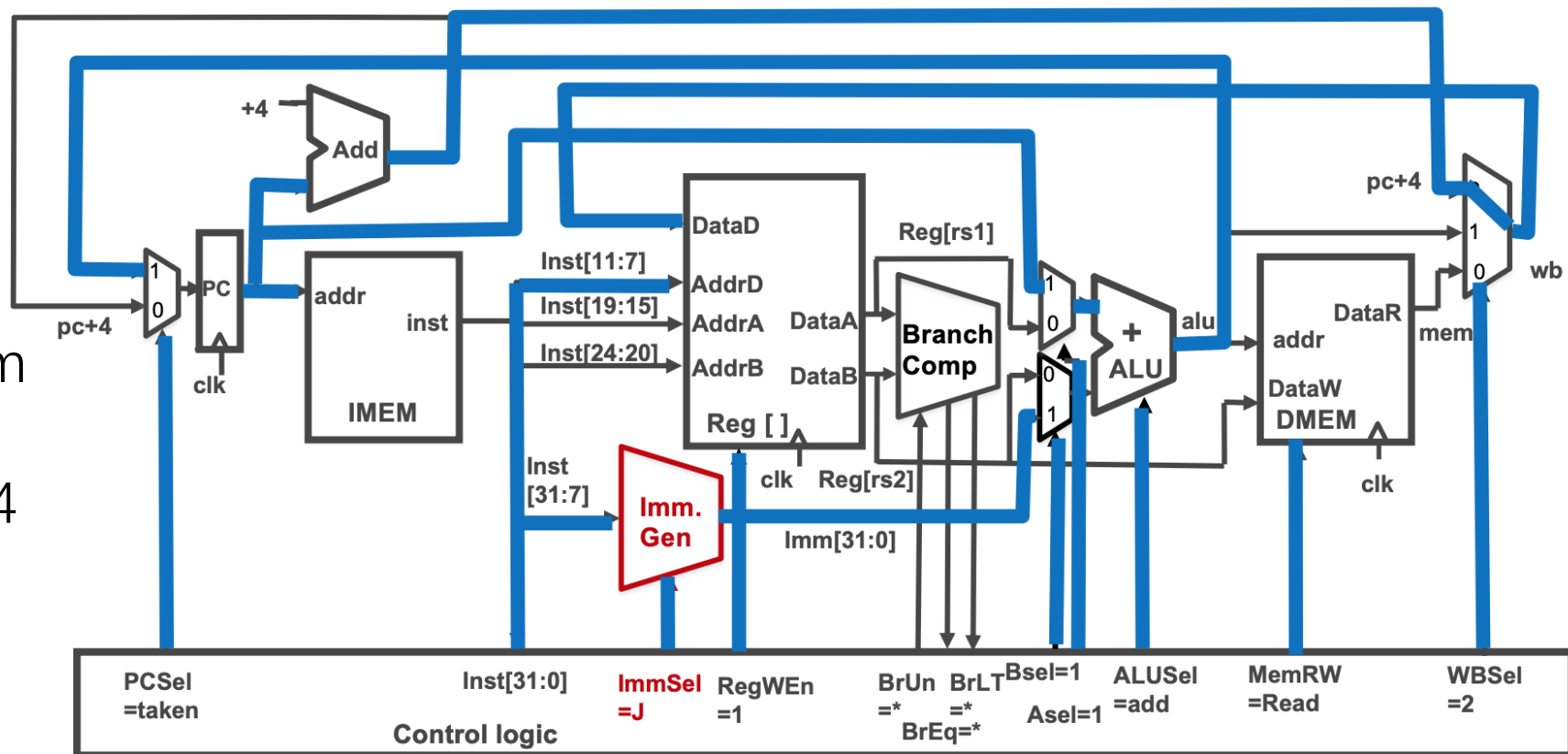- IF
- ID
- EX: $alu = PC + imm$
- ~~MEM~~
- WB: $R[rd] = PC + 4$
- $PC = alu$



U-format: auipc

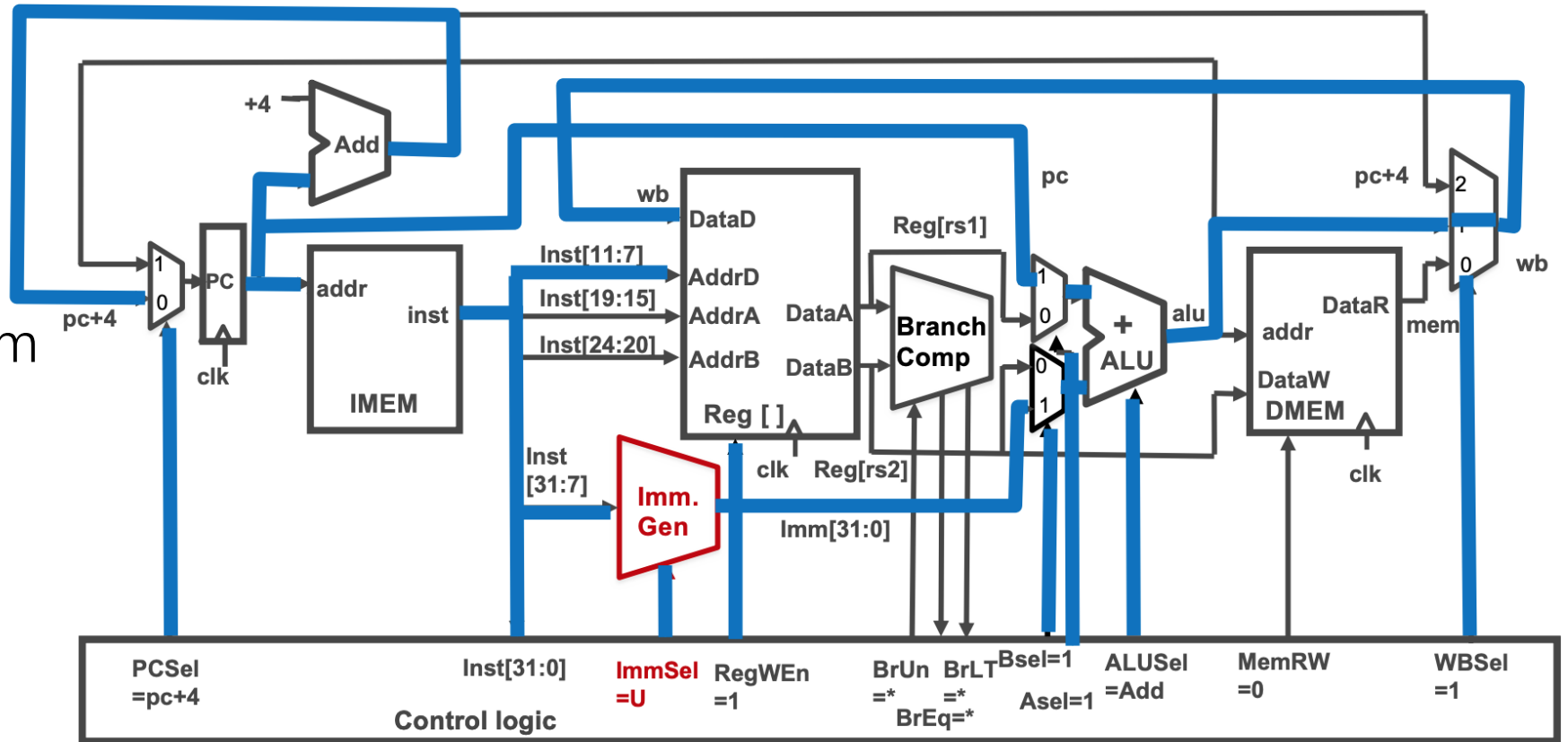- IF
- ID
- **EX**: $alu = PC + imm$
- ~~MEM~~
- **WB**: $R[rd] = alu$
- $PC = PC + 4$



Example from CA 2022 final

For instruction `jalr ra`, select the correct value for the control logic.

1. PCSel:


- A. alu
- B. $pc + 4$

2. Asel:

- A. 0
- B. 1

3. WBsel:

- A. $pc + 4$
- B. alu
- C. mem

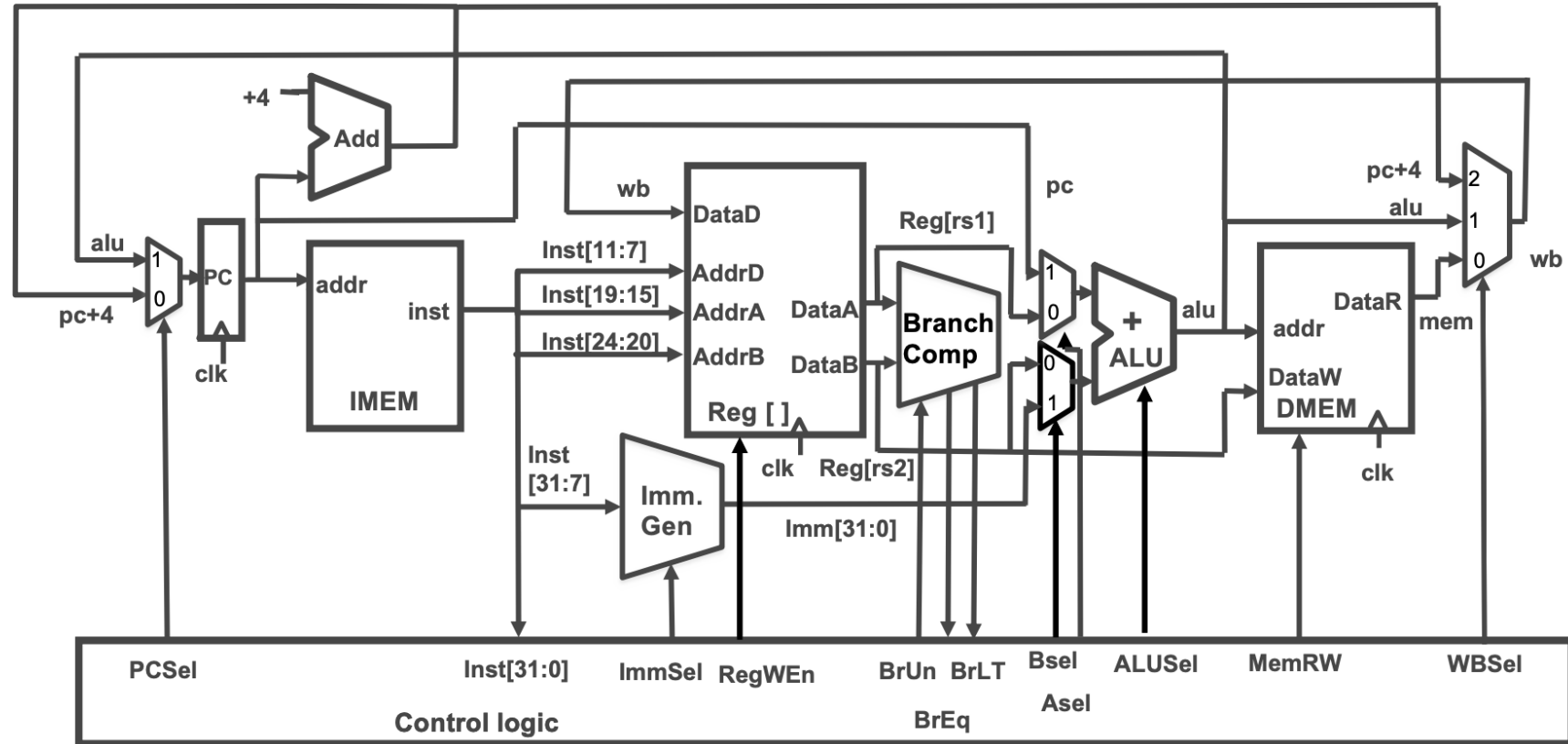

Example from CA 2022 final

For instruction `jalr ra`, select the correct value for the control logic.

1. PCSel:

A. alu

B. $pc + 4$

2. Asel:

A. 0


B. 1

3. WBsel:

A. $pc + 4$

B. alu

C. mem

 



Example from CA 2022 final



(True or False)

1. () For instruction add, the value is written back to Reg as soon as it is computed by ALU.
2. () Except Write Enable, all the input and output buses of register file are 32-bit.
3. () For register file and memory, CLK is a factor ONLY during write operation.
4. () Register file holds all the registers needed for instruction execution.



Example from CA 2022 final



(True or False)

1. (**F**) For instruction add, the value is written back to Reg as soon as it is computed by ALU.
2. (**F**) Except Write Enable, all the input and output buses of register file are 32-bit.
3. (**T**) For register file and memory, CLK is a factor ONLY during write operation.
4. (**F**) Register file holds all the registers needed for instruction execution.



Project 2: A RV32C Toy CPU



2.1: Implement CI and CR type instructions

(DDL: May 7th)

Format	ISA	OP[1:0]	Funct3	Implementation
CR	add	10	100	$x[rd] = x[rd] + x[rs2]$
CR	mv	10	100	$x[rd] = x[rs2]$
CI	addi	01	000	$x[rd] = x[rd] + sext(imm)$
CI	slli	10	000	$x[rd] = x[rd] \ll uimm$
CI	li	01	010	$x[rd] = sext(imm)$
CI	lui	01	011	$x[rd] = sext(imm[17:12] \ll 12)$
CI	nop	01	000	None
CSS	swsp	10	110	$M[x[2] + uimm][31:0] = x[rs2]$
CIW	addi4spn	00	000	$x[8+rd'] = x[2] + nzuimm$
CL	lw	00	010	$x[8+rd'] = sext(M[x[8+rs1'] + uimm][31:0])$
CS	sw	00	110	$M[x[8+rs1'] + uimm][31:0] = x[8+rs2']$
CB	beqz	01	110	if $(x[8+rs1'] == 0)$ pc += sext(offset)
CJ	j	01	101	pc += sext(offset)
CJ	jr	10	100	pc = $x[rs1]$

Format	Meaning	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0		
CR	Register	funct4				rd/rs1				rs2				op					
CI	Immediate	funct3		imm		rd/rs1				imm				op					
CSS	Stack-relative Store	funct3		imm						rs2				op					
CIW	Wide Immediate	funct3		imm								rd'		op					
CL	Load	funct3		imm				rs1'		imm		rd'		op					
CS	Store	funct3		imm				rs1'		imm		rs2'		op					
CB	Branch	funct3		offset				rs1'		offset				op					
CJ	Jump	funct3		jump target												op			

Table 1.1: Compressed 16-bit RVC instruction formats.


RVC Register Number	000	001	010	011	100	101	110	111
Integer Register Number	x8	x9	x10	x11	x12	x13	x14	x15
Integer Register ABI Name	s0	s1	a0	a1	a2	a3	a4	a5
Floating-Point Register Number	f8	f9	f10	f11	f12	f13	f14	f15
Floating-Point Register ABI Name	fs0	fs1	fa0	fa1	fa2	fa3	fa4	fa5










Top & testbench




Fixed I/O

 

Don't touch

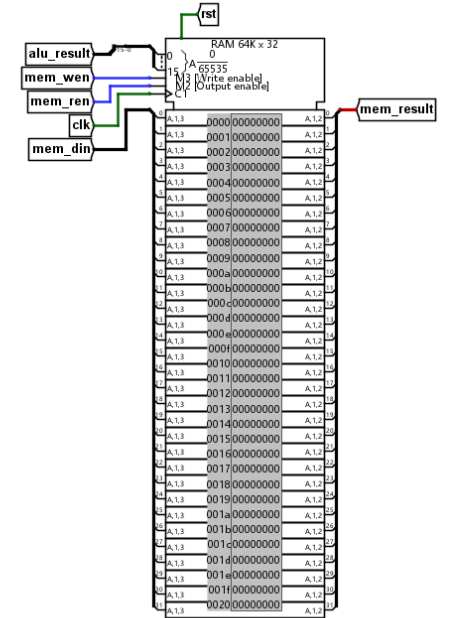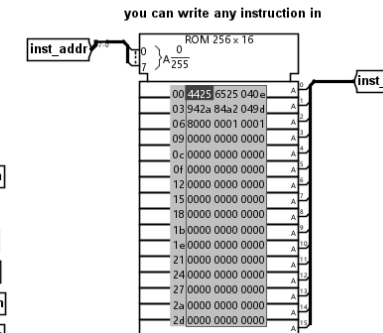 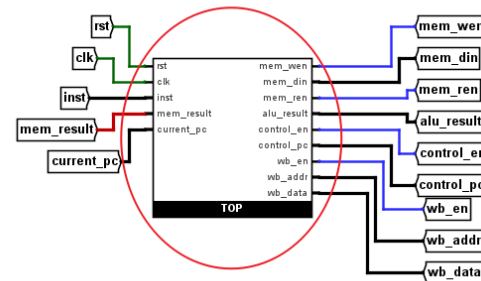  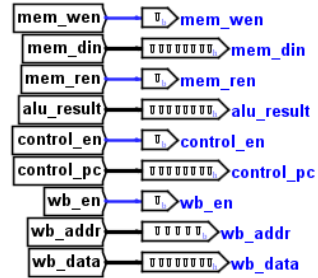

Fetch

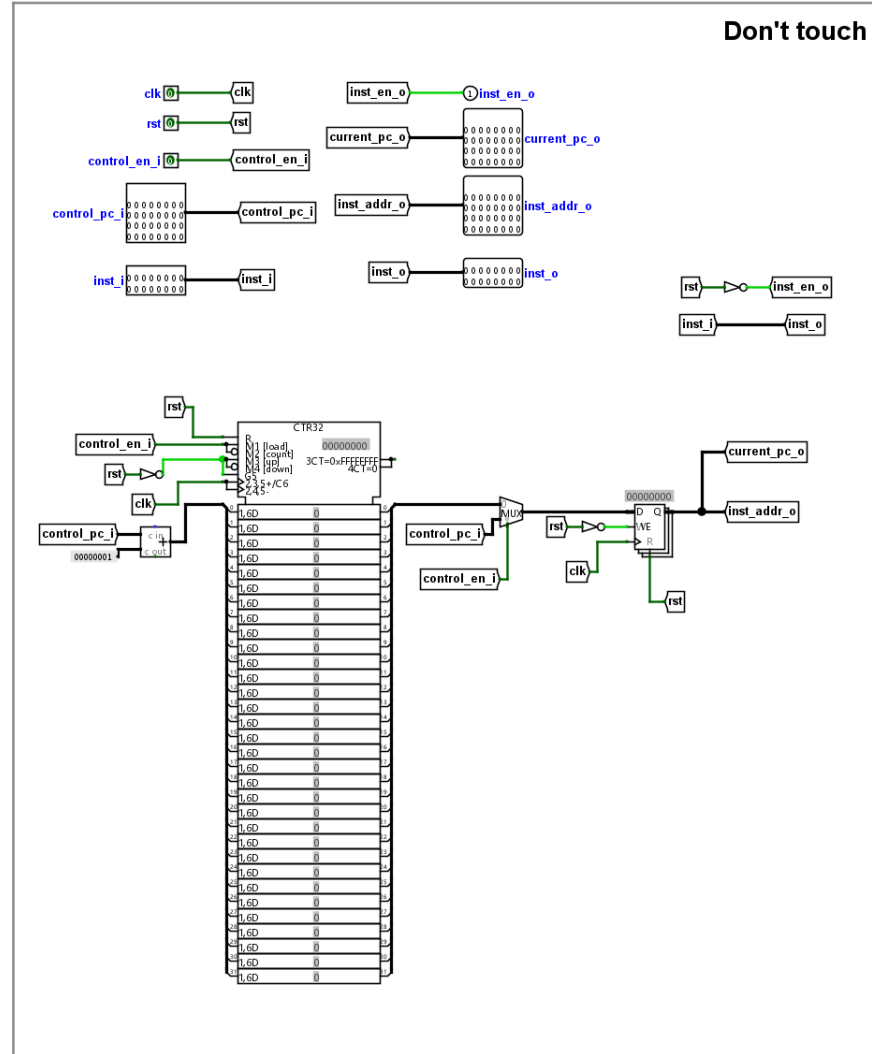

Restriction



- All data is represented in 2's complement form.
- The data memory (RAM) is word-addressable, i.e., each address refers to a 32-bit memory space.
- You should **reset your system** before carrying out any instructions. In other words, during the first cycle, all pins should output **0**.
- To reduce your workload, all test scripts will only involve ten integer registers **x0, x2, x8-x15**.
- All instructions in testcases are valid, and you don't need to consider instruction checking (please note that **NOP** is also a valid instruction in RVC and our CPU).
- Since Logisim supports memory with limited size, only the lower 8 bits of an 32-bit address are used to access instruction memory (ROM) and lower 16 bits to access data memory (RAM).